



Category: Current Source

CIRCUIT IDEAS FOR DESIGNERS

Schematic no. cs_11008.1

High Output Impedance Cascode Current Mirror

Description

This current source uses a voltage reference and a precision reference resistor that produces an output current that has substantially higher dynamic output impedance, particularly for low current levels of less than 100 μ A. This current source buffers the reference current and produces a constant current for a wide voltage range. This current source utilizes two pairs of N-channel matched pair MOSFETs connected in a cascode configuration. The bottom MOSFET pair must be a matched pair and the top MOSFET pair must also be a matched pair. However, the top pair and the bottom pair do not have to be the same model. The lower voltage compliance range is determined by the 2 x V_{GS}(th) and the upper voltage compliance voltage are limited by breakdown voltage. Use very low V_{GS}(th) devices such as ALD110802 and ALD110800 to reduce the lower voltage compliance limit.

For full schematic diagram and notes, please register and login at aldinc.com

©2005 Advanced Linear Devices, Inc. Information furnished by Advanced Linear Devices, Inc. (ALD) is believed to be accurate and reliable. However, ALD assumes no responsibility for the use of such information nor for any infringement of patent or rights of third parties that may result from its use. No license is granted implication or otherwise under any patent rights of ALD.