



Category: Voltage Follower

CIRCUIT IDEAS FOR DESIGNERS

Schematic no. vf_27002.0

Micropower Buffered Rail-to-Rail Adjustable Voltage Source

Description

This circuit is a variation to the basic connection of a unity gain buffer amplifier. The unity gain amplifier is used primarily to isolate the input from the output. In this configuration, the output is connected back to the negative input terminal of the amplifier. Therefore any voltage at the output would be forced upon the -ve input as well. As the operational amplifier has very high open loop gain, the output voltage would tend to be forced to a value very close to VIN voltage. Any difference in voltage between the +ve input and the -ve input terminals would result in an equivalent input voltage applied across the inputs of the operational amplifier, which is then amplified by the open loop gain of the operational amplifier. By using a rail-to-rail operational amplifier (see list below), the input voltage VIN can be at any voltage between the V+ and V- supply rails. The output of the rail-to-rail operational amplifier generally has a very low output resistance, which, when connected to a load resistor, would result in an output voltage that can reach from within a few millivolts to a few tenths of millivolts from the supply rails. The actual output voltage achievable depends on the output impedance of the operational amplifier (RIN >~ 1000 Gohm). Generally a potentiometer 1 Mohm or higher is used to limit the power consumption across the potentiometer.

For full schematic diagram and notes, please register and login at aldinc.com

©2005 Advanced Linear Devices, Inc. Information furnished by Advanced Linear Devices, Inc. (ALD) is believed to be accurate and reliable. However, ALD assumes no responsibility for the use of such information nor for any infringement of patent or rights of third parties that may result from its use. No license is granted implication or otherwise under any patent rights of ALD.