



## Category: Waveforms & Filters

## CIRCUIT IDEAS FOR DESIGNERS

Schematic no. wf\_47001.0

**Micro-power Band-pass Network** 

## Description

This circuit utilizes an operational amplifier with relatively high slew rate per unit power consumption configured as a band-pass filter circuit. The input is ac coupled with the low frequency cutoff point determined by R1C1. The feedback network cutoff at a high frequency determined by R2C2. Start the operational amplifier selection process by determining a) the available voltage supplies; b) the high frequency response time required; c) the offset voltages required. An operational amplifier with very high input impedance (a few pA input currents) and an output settling time specification, such as the ALD1704, would help to implement the filter while minimizing other unexpected surprises, such as ringing within the band. If the power consumption of the operational amplifier is important, select an operational amplifier with the maximum slew rate per unit current consumed that would be just adequate for the frequency range of interest. Having selected a suitable limited bandwidth operational amplifier with docile settling characteristics, such as the ALD1702, calculate if the necessary gain bandwidth of the operational amplifier would be adequate for the band-pass range required.

For full schematic diagram and notes, please register and login at aldinc.com

©2005 Advanced Linear Devices, Inc. Information furnished by Advanced Linear Devices, Inc. (ALD) is believed to be accurate and reliable. However, ALD assumes no responsibility for the use of such information nor for any infringement of patent or rights of third parties that may result from its use. No license is granted implication or otherwise under any patent rights of ALD.