



Category: SABFET

CIRCUIT IDEAS FOR DESIGNERS

Schematic no. sabfet_11103.0

Balancing 3-Supercap Cells in Series**Description**

Three MOSFETs of a quad supercapacitor auto balancing (SAB) MOSFET array connects across three-supercaps in series, using the ALD 8100xx series, with xx equal to the threshold voltage, V_t , in 0.10V increments. At V_t , the I_{DS} ON current for each SAB MOSFET M1/M2/M3 is set at $1\mu\text{A}$. The I_{DS} ON current of M1/M2/M3 change exponentially with slight changes in the gate-source voltage, V_{GS} . Each SAB MOSFET M_x behaves like a voltage sensitive resistor (See sabfet_11101.0). At V_{GS} voltages below or above V_t , the SAB MOSFET I_{DS} ON current changes at a rate of approximately 1 decade for every 0.1V change in V_{GS} . When V_{GS} drops low enough, the I_{DS} ON current becomes essentially zero. For example, the ALD810025 has a V_t of 2.50V. If its V_{GS} voltage falls below 1.9V, the I_{DS} current decreases to pA range, which is near zero compared to $1\mu\text{A}$.

The voltages across M1/M2/M3 automatically self-adjust to accommodate different leakage currents for each supercap C1/C2/C3. V_1 and V_2 settle to approximately $2/3 (V_+)$ and $1/3 (V_+)$ respectively, depending upon relative leakage currents of each supercap in the stack. The currents through M1/M2/M3 automatically compensate for different supercap voltages. A higher supercap voltage results in a higher corresponding V_{GS} voltage of M_x connected across it, at a higher I_{DS} ON current, which opposes the tendency for the higher supercap voltage to increase. A lower supercap voltage results in lower I_{DS} ON currents in the corresponding SAB MOSFET until I_{DS} ON ≈ 0 . In equilibrium, the total leakage current across both M1/M2/M3 and C1/C2/C3 network is approximately equal to the highest leakage current of any one of C1/C2/C3.

For full schematic diagram and notes, please register and login at aldinc.com