



## Function Generator

### Description

This circuit utilizes a quad operational amplifier to produce 4 outputs at the 4 stages, consisting of a square wave output, a triangle wave output, a sine wave output and  $-2X$  gain amplifier respectively. The first stage functions as a square wave generator. Initially, assume that its output is at  $V+$  (+2.5V). The +input voltage is determined by the ratio of the resistor divider, which, in this case, are the 27K and the 100K resistors. The output signal feeds back to +ve input terminal via the resistor network, with the operational amplifier acting as a comparator. A RC network charges the capacitor at -ve input terminal until the voltage crosses that at the +input voltage. At that point the output of the amplifier changes state to  $V-$  (-2.5V) as a result of amplifying now a negative input signal. The voltage on the +ve input terminal changes to a negative of the resistor divider ratio voltage. The RC network begins to discharge toward  $V-$ . When the voltage at -ve input terminal crosses below +ve input voltage, the output flips again to  $V+$ . Therefore the circuit functions as an oscillator, generating a square wave. When this square wave is integrated at the second stage, a triangle wave is generated at the output. Another integration of this triangle wave through the third stage produces a sine wave signal at the output of the third stage. The fourth and last stage is merely a standard inverting amplifier with a gain equal to  $-2$ .

For full schematic diagram and notes, please register and login at [aldinc.com](http://aldinc.com)